

Computer Systems – Lab 5

Mohamed Shafi Uzman Fassy

Question 2.

Q2.1 - A clock, an input pin, JK flip flops, D flip flops, and gates, hex displays, and splitters.

Q2.2 - Week 3 content such as shift registers and common clock counter are relevant for the first stage of the alarm clock circuit.

Q3.

